
Problem 3. 12.1)

 $\phi(x) = x^5 + x^2 + 1$

Internal-XOR LFSR

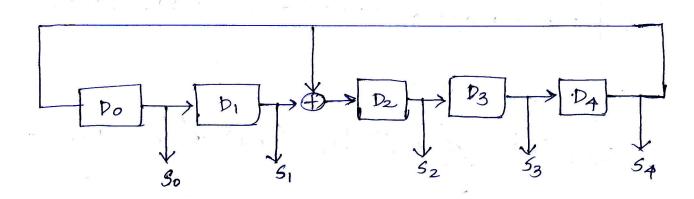

Transition matrix / relation 5(4+1) = A * 5(4)

$$\begin{bmatrix}
S_0(\ell+1) \\
S_1(\ell+1) \\
S_2(\ell+1)
\end{bmatrix} = \begin{bmatrix}
0.00001 \\
100000 \\
0.0001
\end{bmatrix}
\begin{bmatrix}
S_0(\ell) \\
S_1(\ell) \\
S_2(\ell)
\end{bmatrix}$$

$$\begin{bmatrix}
S_0(\ell+1) \\
S_1(\ell) \\
S_2(\ell)
\end{bmatrix}$$

$$\begin{bmatrix}
S_0(\ell+1) \\
S_1(\ell) \\
S_2(\ell)
\end{bmatrix}$$

$$\begin{bmatrix}
S_0(\ell) \\
S_2(\ell)
\end{bmatrix}$$

$$\begin{bmatrix}
S_0(\ell) \\
S_1(\ell)
\end{bmatrix}$$

$$\begin{bmatrix}
S_0(\ell) \\
S_1(\ell)
\end{bmatrix}$$

$$\begin{bmatrix}
S_0(\ell) \\
S_2(\ell)
\end{bmatrix}$$

$$\begin{bmatrix}
S_0(\ell) \\
S_1(\ell)
\end{bmatrix}$$

$$\begin{bmatrix}
S_0(\ell$$

Initial seed

Cyclic repetition

2

Sequence generated at the output of the last stage of the LFSR. = 54 =

using equation 12.4

(n-1) $n-i \left[s_{n-1} \left(-n+i \right) + s_{n-1} \left(-n \right) \right]$ (a6-1) $(x) = \sum_{i=0}^{n-1} \phi_i x^{i} \left[s_{n-1} \left(-n+i \right) + s_{n-1} \left(-n \right) \right]$

can be rewritten as $G_{in-1}(x) = \frac{1}{1+\sum_{i=0}^{(n-1)} \phi_i x^{n-i}}$

$$\Rightarrow G_{n-1}(x) = \frac{1}{x^n \phi(1/x)} =$$

$$\Rightarrow G_{n-1}(x) = \frac{1}{x^5 \left[\left(\frac{1}{2} \right)^5 + \left(\frac{1}{2} \right)^2 + 1 \right]}$$

$$=\frac{1}{1+x^3+x^5}$$

$$= 1 + x^{3} + x^{5} + x^{6} + x^{7} + x^{10} + x^{11} + x^{12} + x^{13} + x^{17} + x^{18} + x^{20} + x^{21} + x^{22} + x^{24} + x^{26} + x^{31} + x^{21} + x^{21} + x^{22} + x^{24} + x^{26} + x^{31} + x^{21} +$$

using eqn, 12.1

$$G_{1n-1}(x) = \sum_{j=0}^{\infty} S_{n-1}(j)x^{j}$$

3


comparing $G_A(x) = \frac{8}{5} \cdot 5_A(j)x^j$

The coefficient of xj in Ga(x) are 54(j).


-. SA = [10010110011111000110111010100001]

Here the two sequences are identical.

12.8)

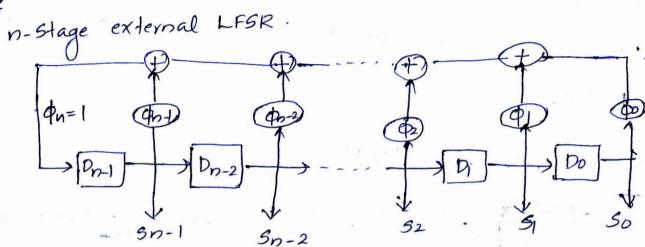

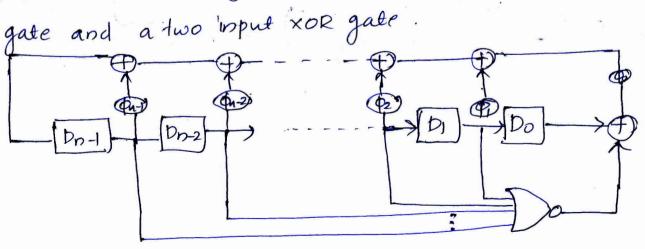
To generate a complete set of n-bit PTVs, the LFSR can be modefied by the addition of an (n-1) input NOR





→ when LFSR has 0.000, the output of NOR is I again but the last XOR injects a 1, so the next state will be out of all zero state.


2. This way we can generate a complete set of n-bit PTV 5.

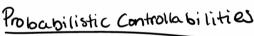12.13 Estimate probabilistic controllabilities and observability for each line in the circuit shown in Figure 4.24(a) using the circuit traversal approach. Use the above values to obtain an estimate of the detectability profile for this circuit.



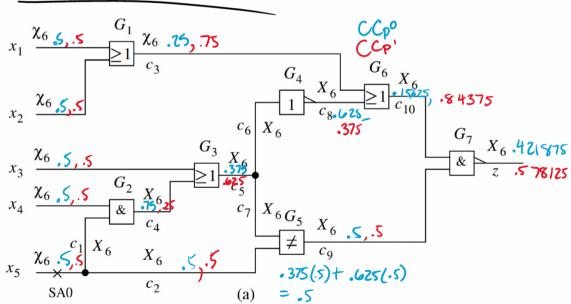

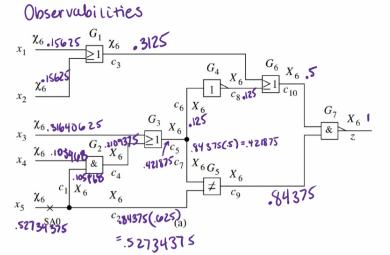

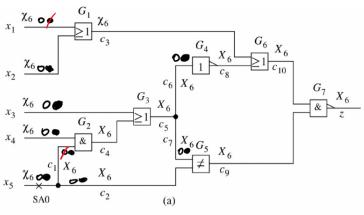

 $-D_p(f) = CC_p^{-1}(c_i)O_p(c_i)$, if f is an SA0 fault at c_i $-D_p(f)=CC_p^0(c_i)O_p(c_i)$, if f is an SA1 fault at c_i $\kappa_f = 2^n \cdot D_p(f)$.

X1 sa0

- Dp = .5*.15625 = 0.07813
- Kf = 2^5*.07813 = 2.50016

X2 sa0

- Dp = .5*.15625 = 0.07813
- Kf = 2^5*.07813 = 2.50016

X2 sa1

- Dp = .5*.15625 = 0.07813
- Kf = 2^5*.07813 = 2.50016

X3 sa0

- Dp = .5*.31640625 = 0.15820313
- Kf = 2^5*.15820313 = 5.06250016

X3 sa1

- Dp = .5*.31640625 = 0.15820313
- Kf = 2^5*.15820313 = 5.06250016

X4 sa0

- Dp = .5*.107187 = 0.053594
- Kf = 2^5*.053594 = 1.715008

X4 sa1

- Dp = .5*.107187 = 0.053594
- Kf = 2^5*.053594 = 1.715008

X5 sa0

- Dp = .5*.52734375 = 0.26367188
- Kf = 2^5*.26367188 = 8.43750016

X5 sa1

- Dp = .5*.52734375 = 0.26367188
- Kf = 2^5*.26367188 = 8.43750016

C1 sa1

- Dp = .5*.107187 = 0.053594
- Kf = 2^5*.053594 = 1.715008

c2 sa0

- Dp = .5*.52734375 = 0.26367188
- Kf = 2^5*.26367188 = 8.43750016

c2 sa1

- Dp = .5*.52734375 = 0.26367188
- Kf = 2^5*.26367188 = 8.43750016

C6 sa0

- Dp = .625*.125 = 0.0781
- $Kf = 2^5*.0781 = 2.4992$

C6 sa1


- Dp = .375*.125 = 0.0469
- Kf = 2^5*.0469 = 1.5008


- Dp = .625*.421875 = 0.263672
- Kf = 2^5*.263672 = 8.437504

C7 sa1

- Dp = .375*.421875 = 0.158203
- Kf = 2^5*.158203 = 5.062496

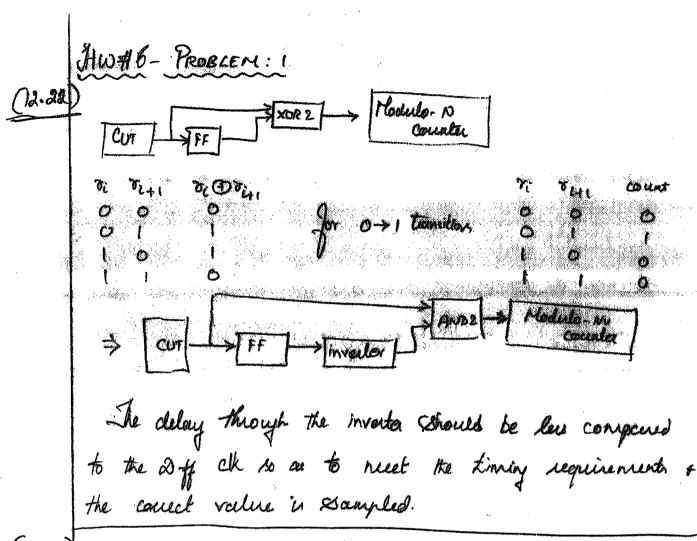 $H = \{h2.5 = 4, h5 = 3, h1.7 = 3, h8.43 = 5, h1.5 = 1\}$



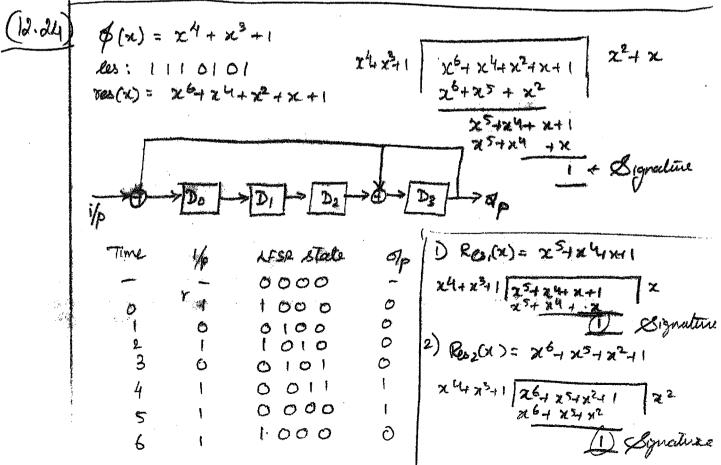

12.25 The MISR sequence can be obtained by XOR aperations as follows:

 e_{11} e_{12} --- e_{1m} e_{21} e_{22} -- e_{2m-1} e_{2m}

MISR segnence & length Ny+n-1

No > no of vectors

n > no of bils for each MISR output

To obtain an all-zero MISR sequence, the output of each XOR operation (each estumn) must be equal to 0.

- (1) Now, for a column k with an infut, The \times OR g a_{K} uiputs will result in an output g O A on $\left(\frac{1}{2} \times 2^{a_{K}}\right)$ occasions.
- (2) Out 3 M, +m-1 columns. (the length of MISR sequence), there are (m-NV+1) columns with NV injule to the XOR operation

The no. of combinations of the (m-Nv+1) columns to have a zero output for their respective $\times 0R$ operation \overline{u} : $C_1 = \left(\frac{1}{2} \times 2^{Nv}\right)^m - Nv+1 = 2^{(Nv-1)}(m-Nv+1)$

For the remaining columns, the no of possible combinations to obtain an all-zuo amas XOA output is:

Rene columns = (M+m-1) - (m-Nv+1)= 2(Nv-1)C. e (Nv-1) on delter side g (m-Nv+1) columns No g possibilitie

$$C_{2} = \left[\left(\frac{1}{2} \times 2^{1} \right) \times \left(\frac{1}{2} \times 2^{2} \right) \left(\frac{1}{2} \times 2^{3} \right) \cdot \cdot \cdot \cdot \left(\frac{1}{2} \times 2^{(N_{N}-1)} \right) \right]^{2}$$

$$= 2^{\left(\frac{N_{N}-1}{2} \right) N_{N}} \cdot \left(\frac{1}{2} \right)^{N_{N}-1} \cdot 2^{\left(\frac{N_{N}-1}{2} \right) \left(\frac{N_{N}-1}{2} \right) \cdot \left(\frac{1}{2} \times 2^{(N_{N}-1)} \right) \cdot \left(\frac{1}{2} \times 2^{(N_{N}-1)} \times 2^{(N_{N}-1)} \right) \cdot \left(\frac{1}{2} \times 2^{(N_{N}-1)} \times 2^{(N_{N}-1)} \right) \cdot \left(\frac{1}{2} \times 2^{(N_{N}-1)} \times 2^{(N_{N}-1)} \times 2^{(N_{N}-1)} \right) \cdot \left(\frac{1}{2} \times 2^{(N_{N}-1)} \times 2^{(N_{N$$

i. Total number q possible combinations to solain an all-zero MISK seguence

$$N = C_1 \cdot C_2$$
= $2^{(NN-1)(m-NV+1)} \cdot 2^{(NV-1)(NV-2)}$
= $2^{(NN-1)(m-NV+1+4NV-2)}$
= $2^{(NN-1)(m-1)}$

A better justification,

etample:

{ m=3 (MISR length) e, ez ez

{ m=5 (#d-pattermsbits fed to MISR)

e, ez ez

e, ez ez Modelements & Column Ny-m+1 column Column Column Column Man 1 23 ...m-1 mm... m m-1.321 A column with ax elements, if we xop them, will generate ofer walf combinations (even #cf 1/2 in it) This means a column with an elements will produce 1/2 camp maxions that if one xCR will preduce ogo, for 3 groups of columns above: $[(k_2^1)(k_2^2)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)-(k_2^m)][(k_2^m)-(k_2^m)-(k_2^m)-(k_2^m)-(k_2^m$ $-\left[\frac{(m-1)m}{2^{m-1}}\right] \left[\frac{(m-1)m}{2^{m-1}}\right] \left[\frac{(m-1)m}{2^{m-1}}\right]$ $= \frac{1}{2^{m-1+N_{v}-N+V+m-V}} \cdot 2$